

EOE-K Scheme (31230) Unit Test-II

2 marks

1. Define unipolar and bipolar devices.
2. What is Oscillator?
3. Define the term Line Regulation with formulae
4. Give the classification of FET.
5. State the need of DC regulated power supply. +
6. Define feedback. State types of feedback.

4 marks

1. Compare between NPN and PNP Transistor.
2. State Barkhausen criteria.
3. Draw the block diagram of DC regulated power supply and describe the working of each block.
4. Draw circuit diagram of Colpitt's oscillator and explain its working.
5. What is switch mode power supply (SMPS) ?
6. Draw the circuit diagram of CB (common base) configuration and draw its input and output characteristics.